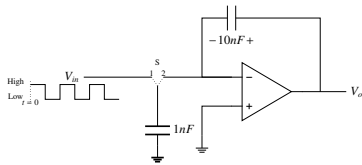


# Gate 2023- Instrumentation Engineering

EE23BTECH11058 - Sindam Ananya\*

**Question 60:** In the circuit shown, the input voltage  $V_{in} = 100mV$ . The switch and the opamp are ideal. At time  $t = 0$ , the initial charge stored in the  $10nF$  capacitor is  $1nC$ , with the polarity as indicated in the figure. The switch  $S$  is controlled using a  $1KHz$  square-wave voltage signal  $V_s$  as shown. Whenever  $V_s$  is 'High',  $S$  is in position '1' and when  $V_s$  is 'Low',  $S$  is in position '2'. At  $t = 20ms$ , the magnitude of the voltage  $V_o$  will be

(GATE IN 2023)



**Solution:**  $0 < t < 0.5ms$

Parameter	Value	Description
$V_{in}$	$100mV$	Input voltage
$q_{10nF}$	$1nC$	Initial charge on $10nF$
$q_{1nF}$		Charge on $1nF$
$f$	$1KHz$	Frequency of $V_s$
$T$	$1ms$	Time period
$V_o$		Output voltage

TABLE 0  
INPUT PARAMETERS

$$q_{1nF} = 100mV \times 1nF \quad (1)$$

$$= 0.1nC \quad (2)$$

$0.5ms < t < 1ms$

Both the capacitors will discharge

$$q_{10nF} = 1nC - 0.1nC \quad (3)$$

$$= 0.9nC \quad (4)$$

At  $t = 20ms$ ,

$$q_{10nF} = 1nC - 20(0.1nC) \quad (5)$$

$$= -1nC \quad (6)$$

$$V_o = \frac{-1nC}{10nF} \quad (7)$$

$$= -100mV \quad (8)$$